

COMP2611: Computer Organization

Introduction to Combinational Logic

- ❑ You will learn about the combinational logic circuits
 - ❑ Do not have internal states (i.e. memoryless),
 - ❑ The output is solely determined by the present input and the circuit,
 - ❑ Can be specified with a truth table or a logic equation (in Boolean algebra expression).
- ❑ Vs Sequential Logic circuits (the next tutorial)
 - ❑ Have memory,
 - ❑ The output depends on both the current input and the value stored in the memory of the circuits (called state).

Combinational logic

Boolean algebra

- review of the Boolean algebra
- the Sum of Product (SoP) representation
- from Boolean algebra to circuit
- PLA implementation
- K-Maps

Exercises

- ❑ The Input-Output relationship of any **combinational logic** circuit can be completely specified using either
 - ❑ a truth table,
 - ❑ or a Boolean algebra expression.
- ❑ When there are N inputs, the truth table would require as many as 2^N entries.
- ❑ The Boolean algebra expression does not have this “cardinality explosion” problem.

- ❑ Boolean algebra consists of
 - ❑ Boolean variables (with values equal to either '0' or '1'),
 - ❑ and binary operators AND (\cdot), OR ($+$), NOT ($\bar{}$) or ($'$).
- ❑ The AND, OR, and NOT operations form a functionally complete set, as they can specify any logic function.

❑ **Identity laws:**

$$A + 0 = A \quad A \cdot 1 = A$$

❑ **Annihilator (or Zero and one) laws:**

$$A + 1 = 1 \quad A \cdot 0 = 0$$

❑ **Complement laws:**

$$A + \bar{A} = 1 \quad A \cdot \bar{A} = 0$$

❑ **Commutativity laws:**

$$A + B = B + A \quad A \cdot B = B \cdot A$$

❑ **Associativity laws:**

$$A + (B + C) = (A + B) + C \quad A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

❑ **Distributivity laws:**

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C) \quad A + (B \cdot C) = (A + B) \cdot (A + C)$$

□ **Idempotence:**

$$A + A = A \qquad A \cdot A = A$$

□ **Absorption laws:**

$$A + (A \cdot B) = A \qquad A \cdot (A + B) = A$$

□ **De Morgan Laws:**

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

- ❑ Any logic function can be expressed as a two-level representation, either as
 - ❑ the Sum-of-Products (SoP) representation,
 - ❑ or as the Product-of-Sums (PoS) representation.
- ❑ **Example:** Assume the truth table for a circuit is given as:

Inputs		Outputs	
In0	In1	Out0	Out1
0	0	1	0
0	1	1	1
1	0	0	1
1	1	0	0

Express the truth table using SoP representations in Boolean Algebra.


- ❑ For each output (Out0, Out1),
 - I. Observe the rows that the output has a value of '1'.
 - ❑ For Out0, the 1's are at the 1st and the 2nd rows.

In0	In1	Out0
0	0	1
0	1	1

 - II. Write the minterms for the inputs such that the minterms will give 1's for the input patterns in the same rows.
 - ❑ For Out0, the two 1's correspond to the input patterns (in0=0,in1=0) and (in0=0,in1=1). The two minterms that will give 1's are $\overline{\text{in0}} \cdot \overline{\text{in1}}$ and $\overline{\text{in0}} \cdot \text{in1}$
- III. Write the outputs as the OR operation of the minterms found in step two. For Out0, we have $\text{out0} = \overline{\text{in0}} \cdot \overline{\text{in1}} + \overline{\text{in0}} \cdot \text{in1}$


- ❑ By following the above steps. The required expressions for the two outputs (Out0, Out1) are $\text{out0} = \overline{\text{in0}} \cdot \overline{\text{in1}} + \overline{\text{in0}} \cdot \text{in1}$ and $\text{out1} = \overline{\text{in0}} \cdot \text{in1} + \text{in0} \cdot \overline{\text{in1}}$ respectively.
- ❑ Could the expressions for Out0 and Out1 be further simplified using the laws on slide 6?

- ❑ The expression $out0 = \overline{in0} \cdot \overline{in1} + \overline{in0} \cdot in1$ can be viewed as performing the OR operation on two ANDed minterms $\overline{in0} \cdot \overline{in1}$ and $\overline{in0} \cdot in1$.
- ❑ The circuit is as follows. Mind the two AND gates that correspond to the AND expressions and the single OR gate that corresponds to the OR expression.




- ❑ What will be the impact on the circuit if we use the simplified expression (mentioned in the last slide) to build the circuit.

 - Using the same approach, the expression $out1 = \overline{in0} \cdot in1 + in0 \cdot \overline{in1}$ can also be drawn. Combine it with the previous figure we have the overall circuit:



 - The same circuit can be equivalently represented by a **programmable logic array (PLA)** circuit.




- ❑ K-Map is a graphical representation of the truth table or logic function
- ❑ In a K-map each cell represents one possible minterm
- ❑ Cells are arranged following a Gray code i.e., two adjacent cells are such that the corresponding minterms differ in only one variable
- ❑ Simplify expression by finding largest size groups of adjacent cells at 1 in the K-Map
 - ❑ Can only group 2^n adjacent cells where $n = 0, 1, 2, 3, 4, \dots$
 - ❑ Table is a toroid (i.e., rightmost cells are adjacent to the leftmost cells and topmost cells are adjacent to bottom cells)
- ❑ Example: Simplify $F = AB' + AB + A'B$

A \ B	0	1
	0	1
0	$A'B'$	$A'B$
1	AB'	AB

A \ B	0	1
	0	1
0	0	1
1	1	1

$$F = B + A$$

 - ❑ Example: Consider a 7-segment digital display which displays a hexadecimal digit. Each segment is represented by a logic function



- ❑ That is, 4 inputs i_3, i_2, i_1, i_0 to represent values 0, ..., 9, a, b, c, d, e, f (to avoid confusion between 0, and 8 on one hand and D and B respectively, on the other hand, we use miniscule b and d representation)
- ❑ What is the truth table for segment C?
- ❑ Also, use a K-Map to simplify the equation

□ Truth Table for segment C:

	Inputs				Output
Hexadecimal Digit	i_3	i_2	i_1	i_0	C
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	1
B	1	0	1	1	1
C	1	1	0	0	0
D	1	1	0	1	1
E	1	1	1	0	0
F	1	1	1	1	0

□ K-Map:

$i_3 i_2 \backslash i_1 i_0$	00	01	11	10
00	1	1	1	0
01	1	1	1	1
11	0	1	0	0
10	1	1	1	1

□ $C = i_3' i_1' + i_3' i_0 + i_3' i_2 + i_1' i_0 + i_3 i_2'$


Combinational logic

Boolean algebra

- review of the Boolean algebra
- the Sum of Product (SoP) representation
- from Boolean algebra to circuit
- PLA implementation
- K-maps


Exercises

 Question 1: A decoder takes a single N -bit input and outputs 2^N 1-bit signals. The 1-bit output corresponds to the N -bit input bit pattern is true while all other outputs are false. The following figure shows a block diagram for a 2-to-4 decoder.



- Why a 2-bit input can generate 4 outputs in the decoder?
- If the input bits are 11, what will happen to the outputs of the decoder?
- Is it possible to have more than one outputs asserted?
- Name two potential uses of the decoder.
- Implement the decoder using Logisim

 Question 2: A multiplexor is a device that given the control signal, selects one of the inputs to be forwarded to the output. The following figure shows a 4-input multiplexor.



Exercises

- If the inputs A/B are 32-bit in width, what is the data width of the Output O?
- What is the maximum number of inputs if the control signal is 10-bit in width?
- What is the bit-width of the control signal for the multiplexor if there are 9 inputs?

- ❑ Today we have reviewed:
 - ❑ simple Boolean algebra and the related laws,
 - ❑ reducing truth table to the canonical Sum-of-Products form,
 - ❑ converting simple Boolean algebra expressions to circuits,
 - ❑ simple combinational logic circuits,
 - ❑ K-maps.