

# **COMP2611: Computer Organization**

## **Arithmetic Logic Unit**

- ❑ You will learn the following in this tutorial:
  - ❑ the structure of 1-bit MIPS ALUs,
  - ❑ overflow detecting mechanism in the MSB 1-bit ALU,
  - ❑ building a simple 32-bit ALU for the MIPS arithmetic,
  - ❑ implementing the SLT instruction in a 32-bit MIPS ALU.

# Arithmetic Logic Unit

## Review of the 1-bit ALU

- 1-bit ALU
- 1-bit ALU for the MSB
- Overflow detection


## An extended 32-bit ALU

- Ripple carry Add/Sub
- SLT implementation
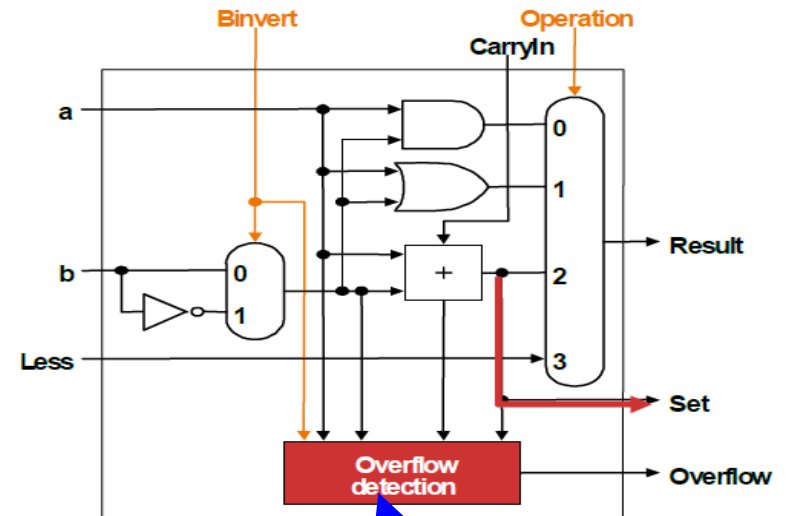
## Exercises

- ❑ 1-bit ALU for bits 0 to 30

- ❑ 1-bit ALU for the Most Significant Bit (MSB): ALU31



## Overflow conditions

Operation	Sign Bit of A	Sign bit of B	Sign bit of Result
A + B	0	0	1
A + B	1	1	0
A - B	0	1	1
A - B	1	0	0

# Arithmetic Logic Unit

Review of the 1-bit ALU


- 1-bit ALU
- ALU for the MSB
- Overflow detection

An extended 32-bit ALU

- Ripple carry Add/Sub
- SLT implementation

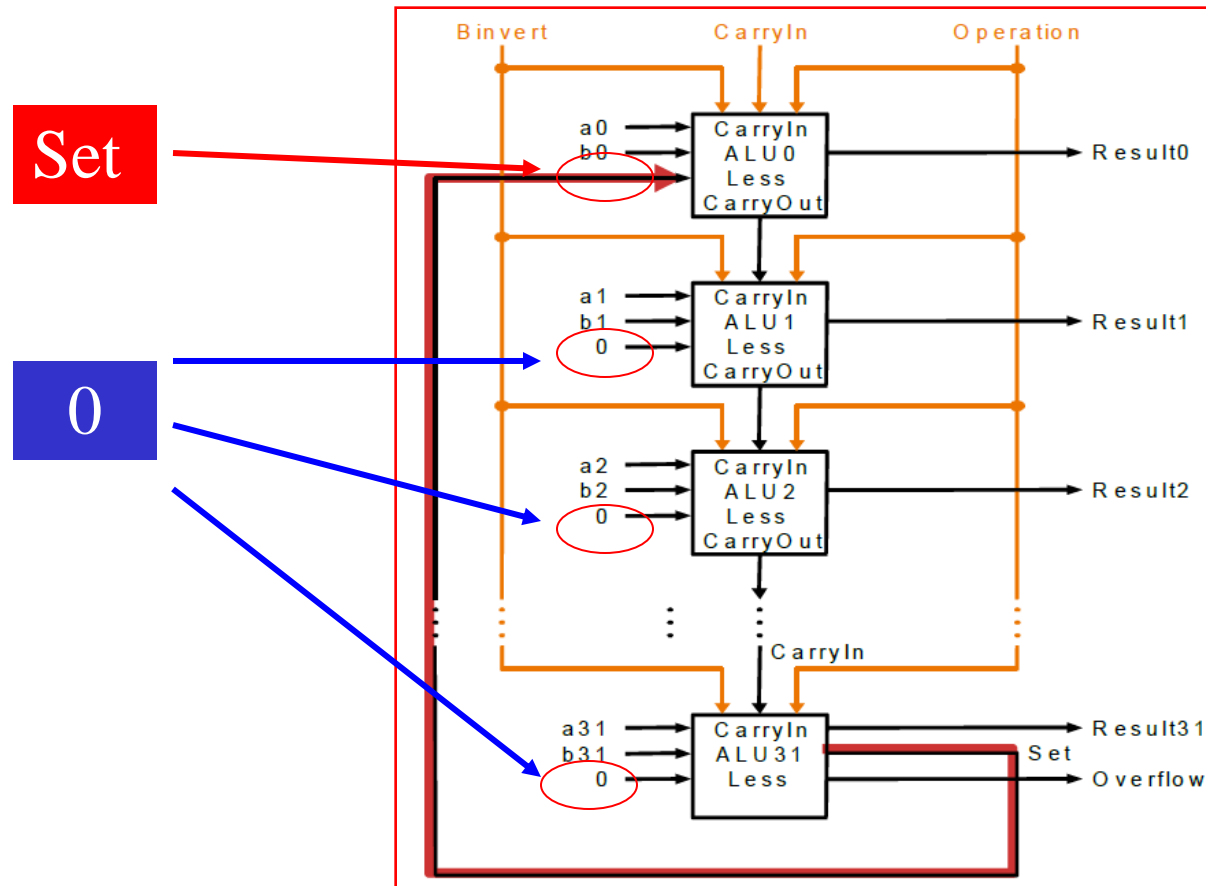Exercises


- ❑ An extended 32-bit ALU (supports SLT) can be formed by connecting 32 1-bit ALUs as follows. Note the 0's at the "Less" input for ALU1-ALU31, note also the **set** signal from ALU31 to ALU0.



	Binvert	CarryIn	Operation
AND	0	X	00
OR	0	X	01
ADD	0	0	10
SUB	1	1	10
SLT	1	1	11

Control signals to ALU0

 **Bnegate** (combine Binvert and CarryIn)



Operation	ALU Control Lines
AND	000
OR	001
ADD	010
SUB	110
SLT	111

Final ALU control lines

# Arithmetic Logic Unit

Review of the 1-bit ALU

- 1-bit ALU
- ALU for the MSB
- Overflow detection

An extended 32-bit ALU

- Ripple carry Add/Sub
- SLT implementation

Exercises




**Question 1:** Some argue that the control signals **Binvert** and **CarryIn** of the bit-0 ALU can be combined into one control signal. Justify this claim (refer to the ALU diagrams on slides 4 and 6 whenever necessary).

**Question 2:** By referring to slides 4 and 6, explain how SLT operation can be performed. State the values for the control signals **Binvert**, **CarryIn** and **Operation**.

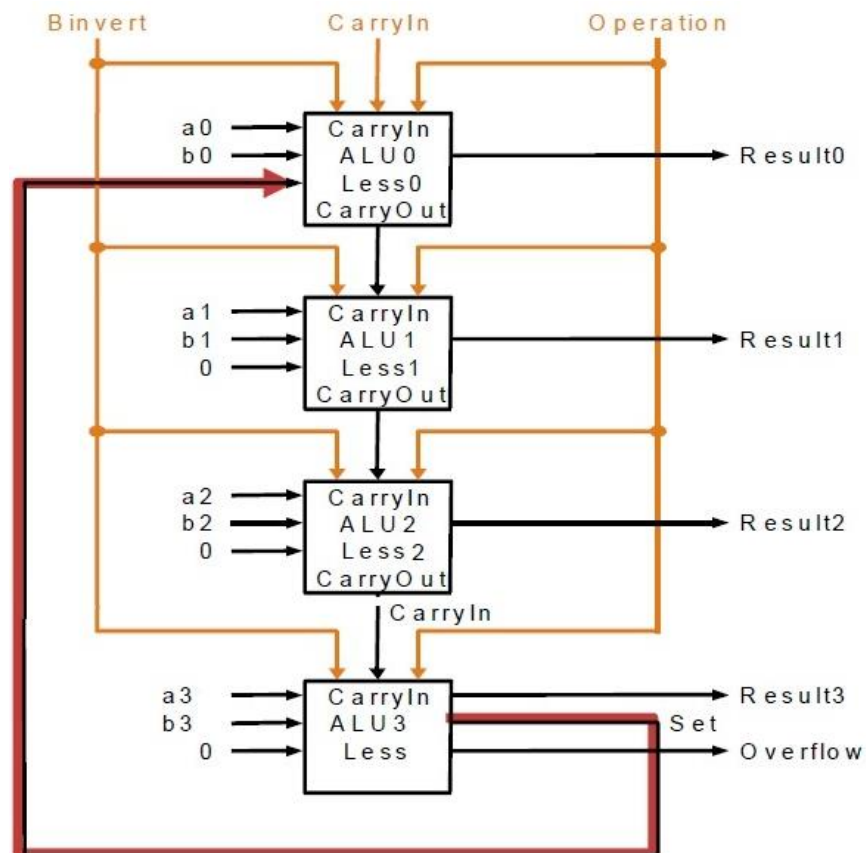**Question 3:** By referring to slides 4 and 6, derive the logic expression in the Sum of Product form (SoP) for overflow conditions based on a 4-bit ALU.

- ❑ **Question 4:** By referring to the 4-bit ALU below, and by filling into the blanks in the table on the next slide, show how the SLT operation is performed. Assume A is 4-bit and is equal to -3, B is also 4-bit and equals to 2.



Solution:

ALU0					Result of Operation			
a0	b0	CarryIn	Binvert	CarryOut	0	1	2	3


ALU1					Result of Operation			
a1	b1	CarryIn	Binvert	CarryOut	0	1	2	3

ALU2					Result of Operation			
a2	b2	CarryIn	Binvert	CarryOut	0	1	2	3

ALU3					Result of Operation			
a3	b3	CarryIn	Binvert	CarryOut	0	1	2	3

**Question 5:** The SLT operation depends on the result of  $A-B$ , and set whenever the sign bit of the operation is asserted. Describe a scenario such that this approach does not work correctly.

 **Question 6:** By referring to the modified 32-bit ALU below, explain how the condition  $A==B$  is detected. State the values for the control signals **Bnegate** and **Operation**.



- ❑ Today we have reviewed:
  - ❑ the structure of 1-bit MIPS ALUs,
  - ❑ overflow detecting mechanism in the MSB 1-bit ALU,
  - ❑ a simple 32-bit ALU for the MIPS arithmetic,
  - ❑ implementing the SLT instruction in a 32-bit MIPS ALU,
  - ❑ implementing the “zero” testing in a 32-bit ALU.